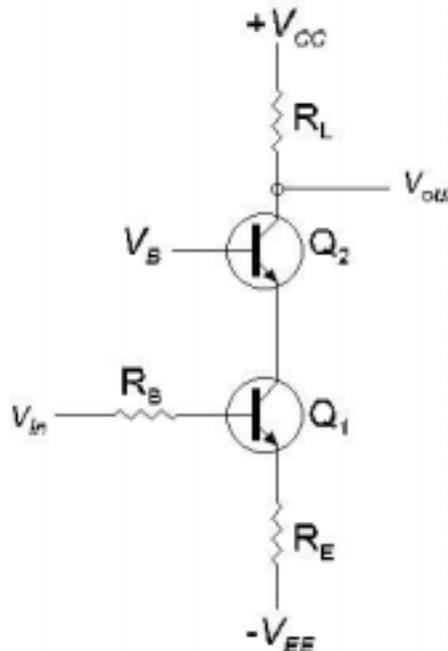


## Cascode Amplifiers

by Dennis L. Feucht

Two-transistor combinations, such as the Darlington configuration, provide advantages over single-transistor amplifier stages. Another two-transistor combination in the analog designer's circuit library combines a common-emitter (CE) input configuration with a common-base (CB) output. This article presents the design equations for the basic cascode amplifier and then offers other useful variations. (FETs instead of BJTs can also be used to form cascode amplifiers.) Together, the two transistors overcome some of the performance limitations of either the CE or CB configurations.

### Basic Cascode Stage



The basic cascode amplifier consists of an input common-emitter (CE) configuration driving an output common-base (CB), as shown above.

The voltage gain is, by the *transresistance method*, the ratio of the resistance across which the output voltage is developed by the common input-output loop current over the resistance across which the input voltage generates that current, modified by the  $\alpha$  current losses in the transistors:

$$A_v = \frac{v_{out}}{v_{in}} = -\alpha_1 \cdot \alpha_2 \cdot \frac{R_L}{R_B / (\beta_1 + 1) + r_{e1} + R_E}$$

where  $r_{e1}$  is  $Q_1$  dynamic emitter resistance. This gain is identical for a CE amplifier except for the additional  $\alpha_2$  loss of  $Q_2$ . The advantage of the cascode is that when the output resistance,  $r_o$ , of  $Q_2$  is included, the CB incremental output resistance is higher than for the CE. For a bipolar junction transistor (BJT), this may be insignificant at low frequencies. The CB isolates the collector-base capacitance,  $C_{bc}$  (or  $C_\mu$  of the hybrid- $\pi$

BJT model), from the input by returning it to a dynamic ground at  $V_B$ . At the output,  $R_L$  is shunted by  $C_{bc}$  only, without a Miller-effect multiplier. The  $Q_1$  collector voltage is also nearly constant and  $C_{bc}$  of  $Q_1$  appears from the input with essentially no Miller effect. The  $C_{bc}$  of the CE has, in the cascode, been isolated from the output and the Miller effect eliminated. This is its primary advantage and is why it is used in fast amplifiers and RF stages.


Another advantage of the cascode over a CE is that the right-half-plane zero that causes preshoot in a step response is also eliminated. In the CE configuration alone,  $C_{bc}$  provides a parallel, passive path from input to output. When a step is applied as  $v_{in}$ , it is coupled to the output node of the CE collector uninverted and precedes the amplified and inverted step as *preshoot*; but not for the cascode. Consequently, the step response of the cascode is not only faster, but "cleaner" than the CE alone.

The cascode incremental output resistance is (with infinite  $r_o$ ) simply  $R_L$ , and the incremental input resistance is, using the  $\beta$  transform:

$$r_{in} = R_B + (\beta_1 + 1) \cdot (r_{e1} + R_E)$$

The resistance in the emitter branch of the input circuit is referred to the base as  $\beta + 1$  times the emitter-side resistance (the  $\beta$  transform), and adds to the base resistance in series with it.


### Complementary Cascode Stage

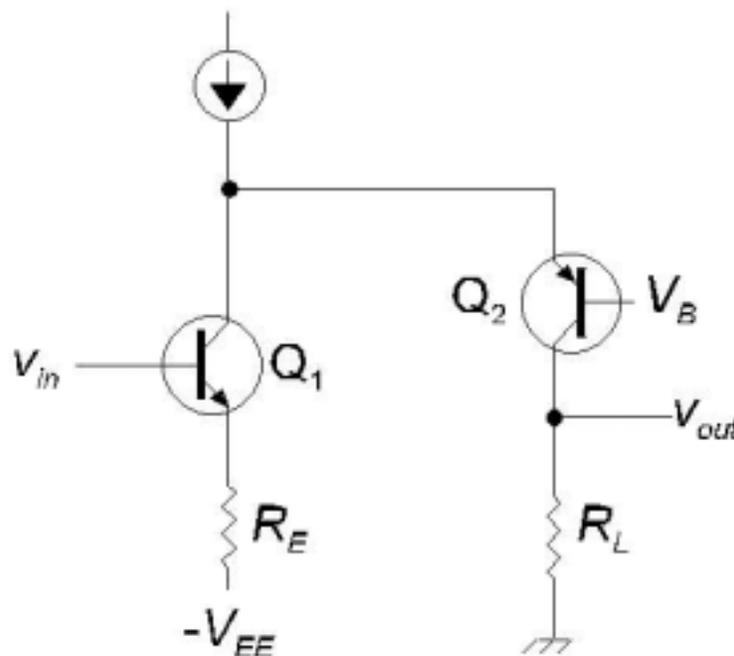

The cascode amplifier also provides voltage translation of the output to a higher static (dc) voltage than the input. This is not always advantageous, however, and can be eliminated by making the CB BJT of opposite polarity to the CE, as shown above.

The output static (dc, quiescent) voltage of the complementary cascode can be the same as the input because the CB BJT inverts the current polarity from the CE. This requires the addition of a bias-current source between the transistors, and the current-source node floats at a junction voltage higher than  $V_B$ . Consequently,  $v_{out}$  can have the same static voltage as  $v_{in}$ , without offset, and the voltage supply used to implement the current source is essentially independent of the rest of the circuit. One implementation is shown below.

By using a current source (consisting of an npn BJT and biasing resistors), a voltage is established across  $R_B$  in series with a diode. The diode compensates for the  $b-e$  junction voltage of  $Q_2$  and tracks it to a first order. Then the voltage drop across  $R_B$  is applied by  $Q_2$  to  $R_C$ . This establishes the static (bias) current shared by  $Q_1$  and  $Q_2$ . For design, the static current of  $Q_1$  is set by  $V_{IN}$ ,  $-V_{EE}$ ,  $V_{BE1}$ , and  $R_E$ . Then the bias current of  $Q_2$  is the difference between the  $Q_1$  current and that of  $R_C$ . The  $Q_2$  static current also sets the static output voltage across  $R_L$ . If  $v_{out}$  should be zero volts with no input applied, then a second resistor from the output node must be returned to  $-V_{EE}$  so that the Thévenin equivalent of the two resistors results in the desired load resistance and equivalent supply voltage.

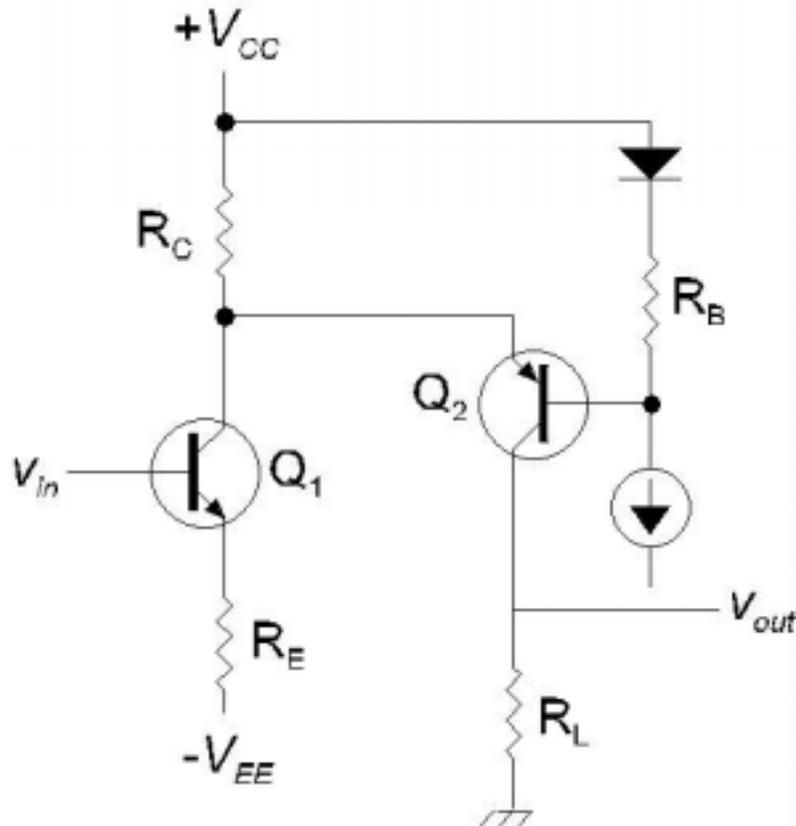


If current biasing is set so that both transistors operate statically at maximum power dissipation then, with a change in input voltage, each will move away from the maximum-power point of operation by approximately the same amount and the resulting thermal distortions will tend to cancel.

A design benefit of the complementary cascode is that the  $Q_1$  collector node can float, along with the base-emitter circuit of  $Q_2$ , at some arbitrarily high voltage, as long as the transistors are rated for it. This amplifier allows op amps or other input sources with low supply voltages to drive the complementary cascode as a high-voltage amplifier. In other words, the output voltage range can far exceed the range of  $v_{in}$  and is not limited by it. As given, the cascode actively drives in the positive-voltage direction from  $Q_2$ . (The "10 A Pulse Amplifier" e-booklet at <http://www.innovatia.com> presents such an amplifier design in detail.)

A differential complementary cascode amplifier, with common (single-node) load resistance at the output can provide a bipolar voltage range. This approach was taken in design of the Tektronix PG508 pulse generator output amplifier, where the complementary-cascode output drives a bipolar emitter-follower to provide output-current capability.
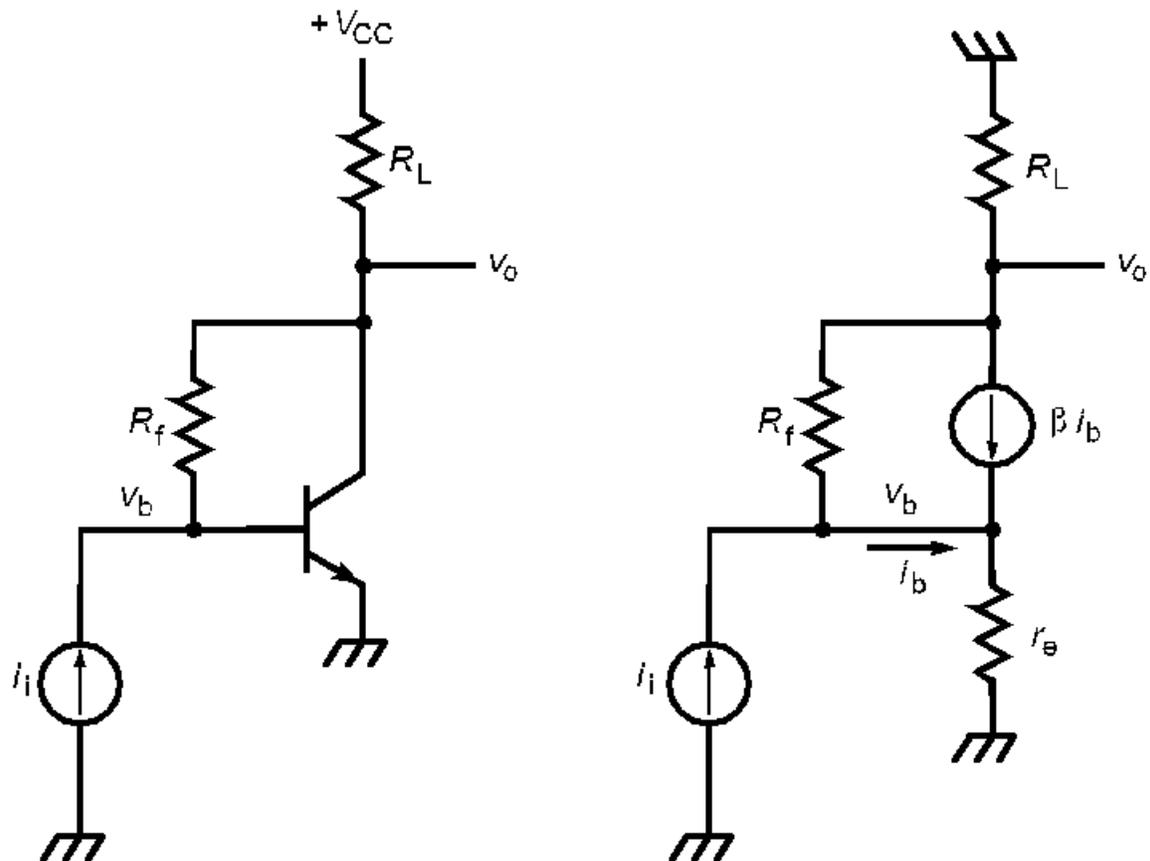
### Shunt-Feedback Cascode Stage

Finally, a variation on the cascode combines it with the shunt-feedback amplifier. The basic shunt-feedback circuit is shown below (left), and with BJT T model (right).



This amplifier will not be explained in detail here. (It is explained in more detail in *Analog Circuit Design*, available from <http://www.innovatia.com> ) It is a transresistance (current in, voltage out) amplifier, with a transresistance of:


$$\frac{v_o}{i_i} = -\alpha \cdot R_f + r_e, R_L \rightarrow \infty$$

if  $R_L$  approaches being a current source (is large relative to  $R_f$ ). For  $R_f \gg r_e$  and  $\alpha \approx 1$ , the transresistance is approximately  $R_f$ . The shunt-feedback amplifier can also be used for high-speed applications. (It has an output impedance equivalent to that of an emitter-follower.) When combined with the cascode, the resulting amplifier - the shunt-feedback cascode - is shown below (a) with incremental (small-signal) model (b).



The transresistance of the shunt-feedback cascode amplifier is:

$$\frac{v_{out}}{i_{in}} = -\alpha_1 \cdot R_1 - \alpha_1 \cdot \alpha_2 \cdot R_2 + r_{e1}$$

$R_1$  in series with  $R_2$  is basically  $R_f$ . Because the current through  $R_2$  loses both base currents before being returned to the input node, both  $\alpha_1$  and  $\alpha_2$  appear in the second gain term. Unlike the simple shunt-feedback stage,  $C_{bc}$  of either BJT does not shunt  $R_f$ , and is divided between transistors. The voltage at the base of  $Q_2$  varies, as the midpoint of an  $R_1, R_2$  voltage divider, and  $Q_2$  is not a purely CB configuration. The two feedback resistor values can be chosen to adjust the extent of the Miller effect across the  $b-c$  junctions of the transistors.

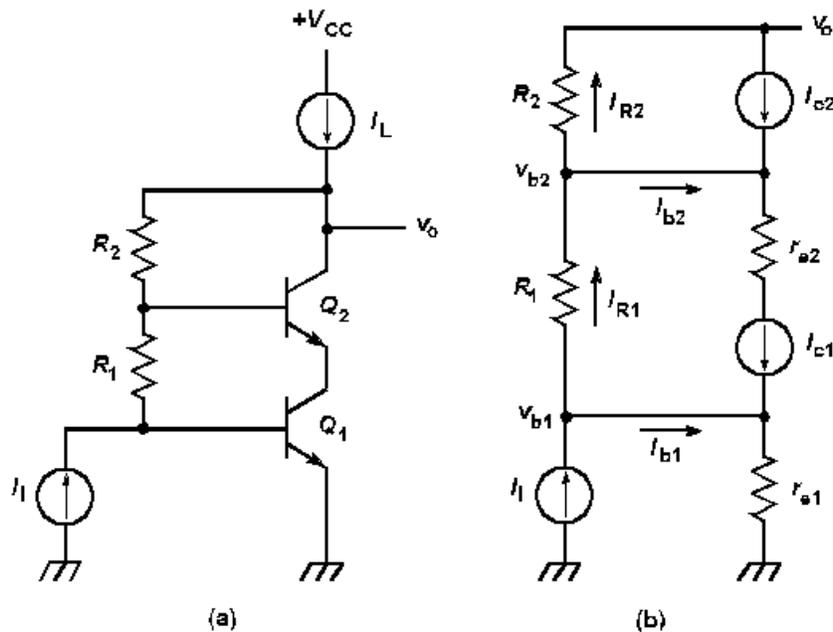

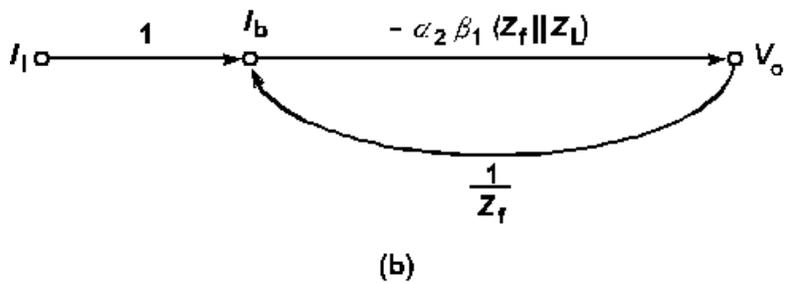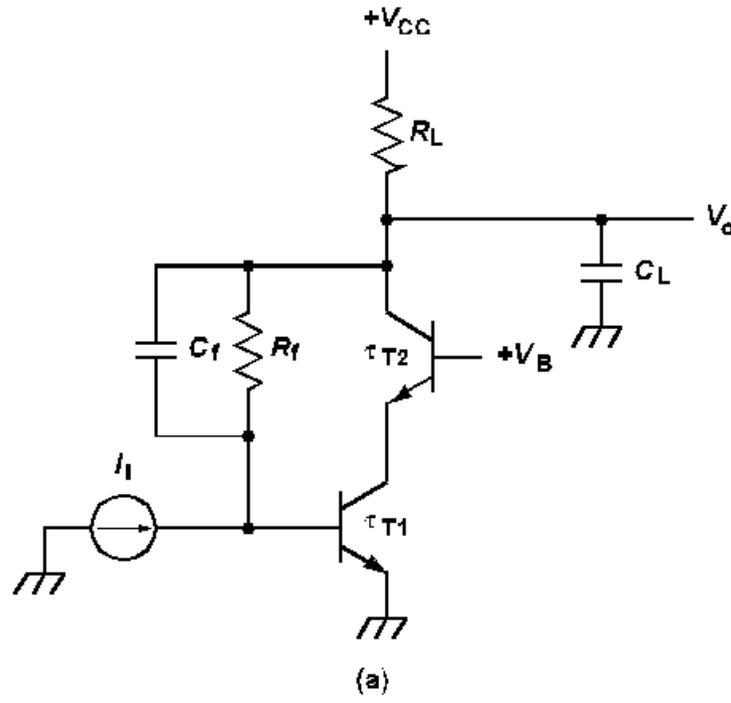If speed is not the driving parameter, but voltage is, then this amplifier provides the advantage of dividing the collector voltage across two series BJTs. If  $R_1 = R_2$ , then each BJT need have only about half the breakdown voltage of a single-BJT amplifier. Again, the cascode shows an advantage for high-voltage applications.



Finally, another shunt-feedback cascode variant uses a single feedback resistor, as shown above in (a), along with a flow graph (for feedback analysis) of the dynamic model of the circuit (b). ( $Z_f$  is  $R_f$  in parallel with  $C_f$  and  $Z_L$  is  $R_L$  in parallel with  $C_L$ .)  $C_f$  is added to provide an additional parameter for adjusting dynamic response. The transistor gain-bandwidth time constant,  $\omega_T$ , is related to  $f_T$  by:

$$\tau_T = \frac{1}{\omega_T} = \frac{1}{2 \cdot \pi \cdot f_T}$$

For  $R_f C_f \gg \tau_{T1}, \tau_{T2}$ , then the poles of the amplifier response follow a circular  $s$ -plane locus as  $\tau_{T2}$  is varied. As  $Q_2$  is made a slower transistor, the closed-loop poles converge, then split off the real axis and follow a circular path to the origin. Variation of  $\tau_{T1}$ ,  $C_f$  or  $C_L$  follows a vertical locus. As any one of them increases in value, the poles move vertically toward the real axis, then split along the axis, heading for the origin and negative infinity.

The dynamic input impedance of this amplifier is interesting. For infinite  $R_f$  and  $\beta_1$ , the input resistance should appear to be infinite but it is not. The *static* input resistance is infinite, but not the *dynamic* resistance. This unusual phenomenon will be the subject of a

future article. (Hint: apply a 1-V step to the input and trace through the effects. As the collector node responds to the input step (but not as a step, because of capacitance), then what is the current through  $C_f$ ? If it is constant, then what impedance does a constant current due to a constant input voltage appear as at the input node?)

### Closure

The cascode amplifier, with its variants, is a basic entry in the circuit designer's library of useful circuits. It has advantages for increasing speed and for high-voltage amplifier applications. For more details on it and other circuits that should be in that library, refer to my 4-volume CD-book, *Analog Circuit Design*, available at <http://www.innovatia.com>

