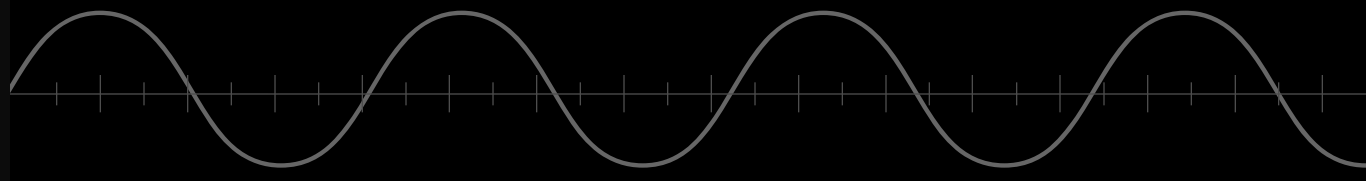


Transformers

Presented by Thomas Mosteller ADI FAE



Ideal Transformer Model

- ❖ Unlike FETs, inductors and so on, there's no transformer model per say in LTspice. To create one:
 - ❖ An inductor must be placed for every transformer winding
 - ❖ The inductors must be coupled together magnetically via the mutual inductance (K) statement placed as a Spice Directive on the schematic
 - ❖ Ex. K1 L1 L2 L3 1
 - ❖ Couple inductors L1, L2 & L3 with a coupling of 1 (ideal transformer)
 - ❖ The turn-ratio is specified by setting the inductor values:

$$L_P/L_S = (N_P/N_S)^2$$
 - ❖ Inductors called out in a "K" statement will be automatically given a phasing dot if one does not already exist.
 - ❖ The "K" directive is specific to a transformer. If more than one transformers are used in a simulation circuit, define a "K" statement for each transformer (K1, K2, ..., K_n)


Ideal Transformers - Lab

Hands-on Exercises:

1.) Open up the file “Transformer2windings.asc” and create   an ideal transformer with the following characteristics:

- ❖ Primary inductance of 100uH
- ❖ A Turn-Ratio (primary-secondary) of 1:3
- ❖ Polarity inversion between the input and output

2.) Modify the previous transformer to add a third winding  (auxiliary) with a 1:2 turn-ratio.


Tip: The use of parameters and equations can simplify the transformer creation process. 

TransformerMultiWindingsWithParamsSolution.as

Leakage Inductances – Two Ways to Model

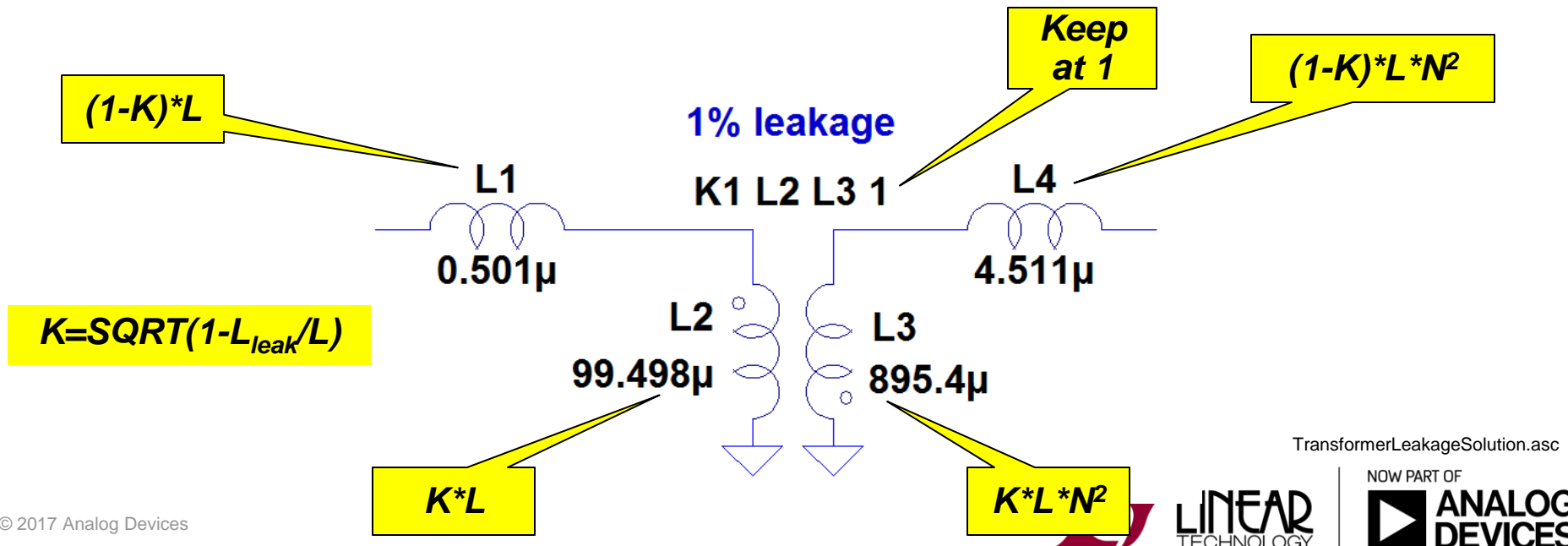1.) Keep the “K” statement to 1:


- ❖ Add a small discrete leakage inductance in series with each winding’s coupled inductance
- ❖ The leakage inductance for each winding will be $(1-K)$ times the inductance of that winding’s inductance.
- ❖ Each winding’s coupled inductance decreases to K times that winding’s inductance
- ❖ Where $K = \text{SQRT}(1 - L_{\text{leakage}}/L)$



Leakage Inductances – Two Ways to Model

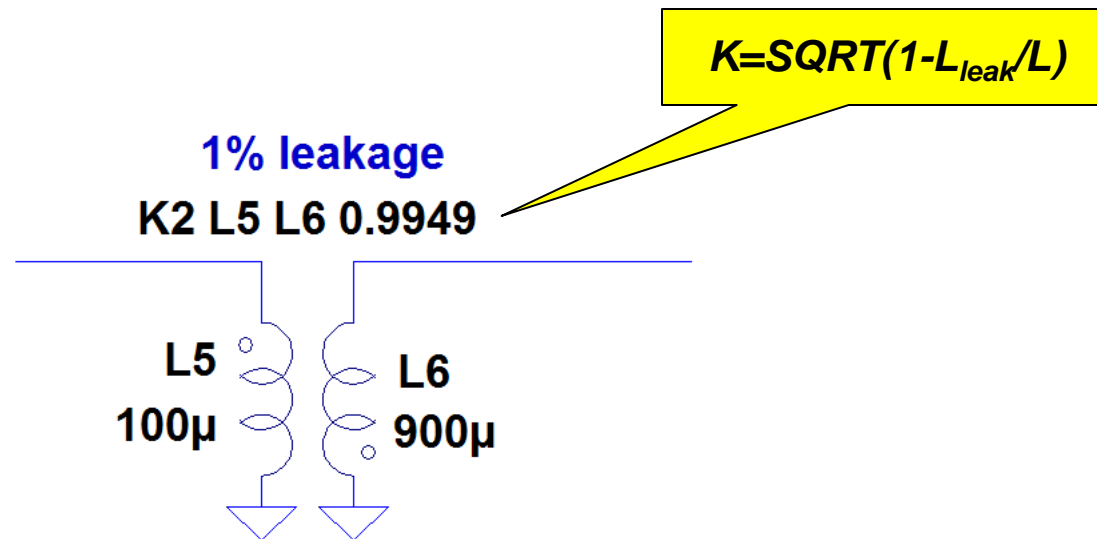2.) Reduce the coupling factor “K” in the “K” statement:

- ❖ Keep the winding’s inductance as if the transformer were ideal
- ❖ Change the “K” statement value to $\text{SQRT}(1 - L_{LK}/L)$
- ❖ The end result will be the same as adding serial inductances.



TransformerLeakageSolution.asc

Appendix

- ❖ LTspice Video channel. “Using transformers” by Gabino Alonso
 - ❖ <http://www.linear.com/solutions/1079>
- ❖ LTJournal – September 2006. “Using Transformers in LTspice” by Mike Engelhardt.
 - ❖ <http://www.linear.com/docs/39380>
- ❖ LTwiki.org. “Transformers” page.
 - ❖ <http://ltwiki.org/?title=Transformers>