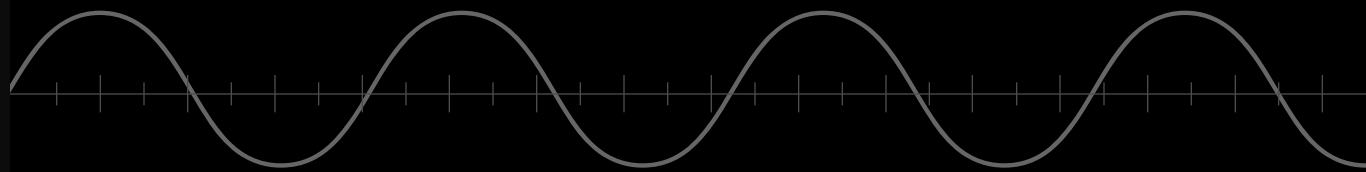


# Voltage & Current Controlled Switches

Presented by Thomas Mosteller



# Voltage Controlled Switch – Model

- ❖ A voltage controlled switch must have a model defined.
  - ❖ Typically done as a SPICE directive placed directly on the schematic
- ❖ The V-switch .model syntax:

```
.model <ModelName> SW(Ron=< $\Omega$ > Roff=< $\Omega$ > Vt=<V> Vh=<V>  
Lser=<H> Vser=<V> Ilimit=<A>)
```

where

*Vt*: Threshold voltage

*Vh*: Hysteresis voltage

*Ron*: On resistance

*Roff*: Off resistance


*Lser*: Series inductance

*Vser*: Series voltage

*Ilimit*: Current limit.
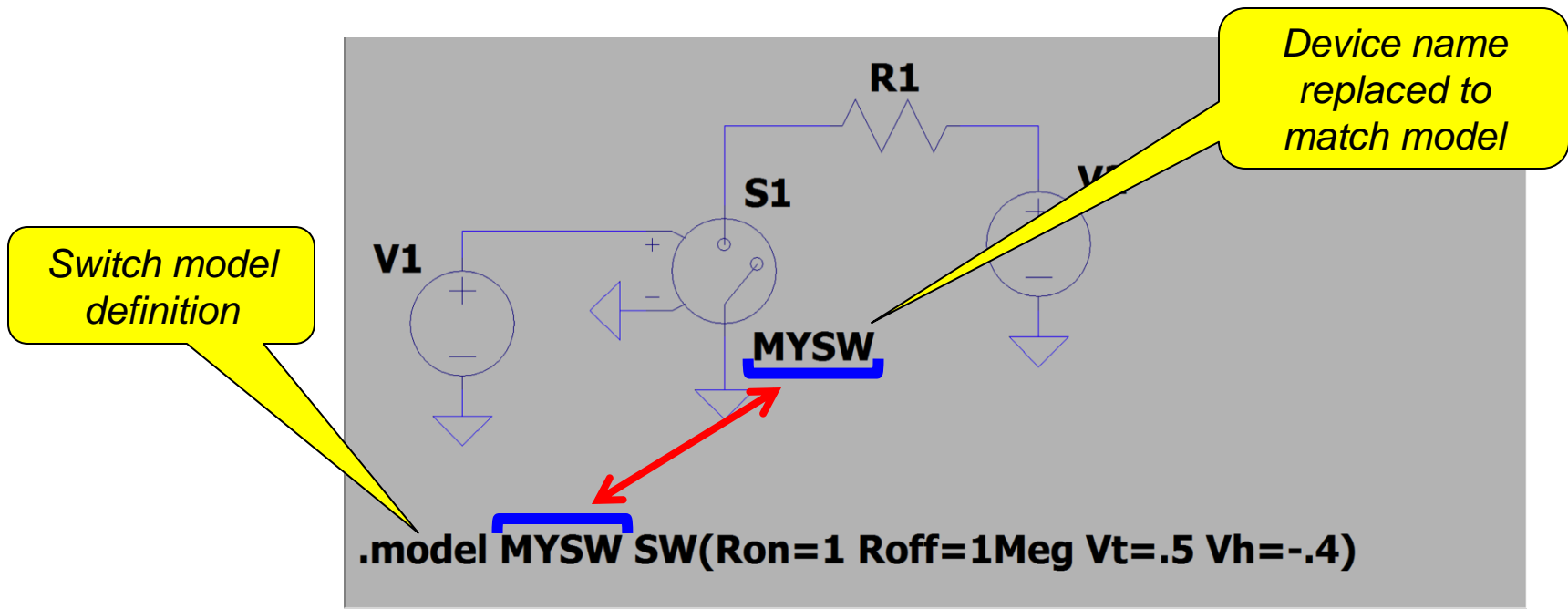
## Voltage Controlled Switch – Model

- ❖ As for other intrinsic Spice models, the device name of the schematic component must be changed to correspond to the switch model name.
- ❖ Schematic example of a voltage controlled switch:



# Voltage Controlled Switch – Modes of Operation


- ❖ The switch has three distinct modes of voltage control depending on the value of the hysteresis voltage,  $V_h$ :
  - ❖  $V_h = 0V$ : Switch is always completely on or off depending upon whether the input voltage is above the threshold.
  - ❖  $V_h > 0V$ : it shows hysteresis, as if it was controlled by a Schmitt trigger with trip points at  $V_t - V_h$  and  $V_t + V_h$ .
    - ❖ Note that  $V_h$  is half the voltage between trip points which is different than the common laboratory nomenclature.
  - ❖  $V_h < 0V$ : it will smoothly transition between the on and off impedances. The transition occurs between the control voltages of  $V_t - V_h$  and  $V_t + V_h$ . The smooth transition follows a low order polynomial fit to the logarithm of the switch's conduction.

# Voltage Controlled Switch
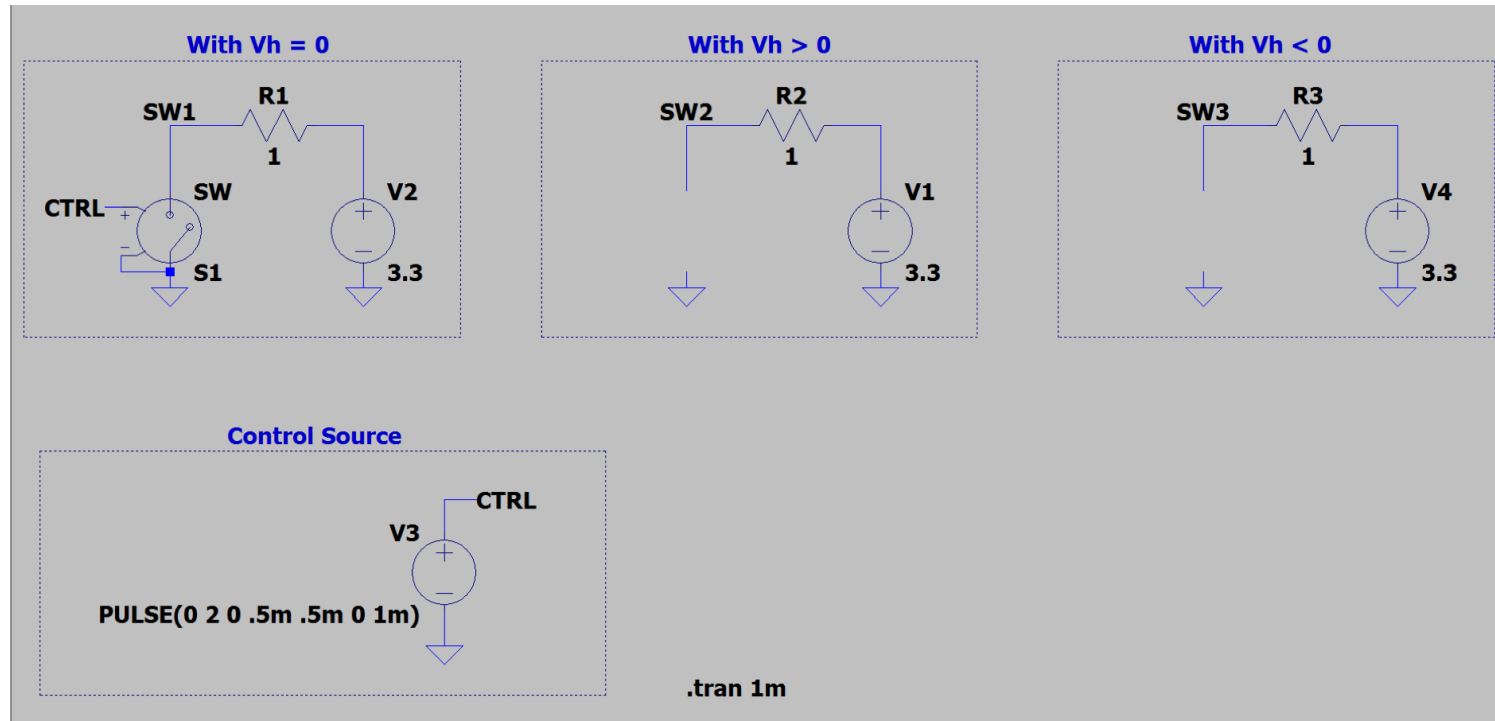
## Hands-on Exercise:



- ❖ Define and use voltage controlled switches.
- ❖ Learn to differentiate the different modes of operation of the V-switch.




# Current Controlled Switch – Model

- ❖ Like the V-switch, the current controlled switch must have a model defined.
  - ❖ Typically done as a SPICE directive placed directly on the schematic
- ❖ The C-switch .model syntax:
  - ❖ *.model <ModelName> CSW(Ron=< $\Omega$ > Roff=< $\Omega$ > It=<A> Ih=<A>)*
    - ❖ The parameters are:
      - It*: Threshold current
      - Ih*: Hysteresis current
      - Ron*: On resistance
      - Roff*: Off resistance

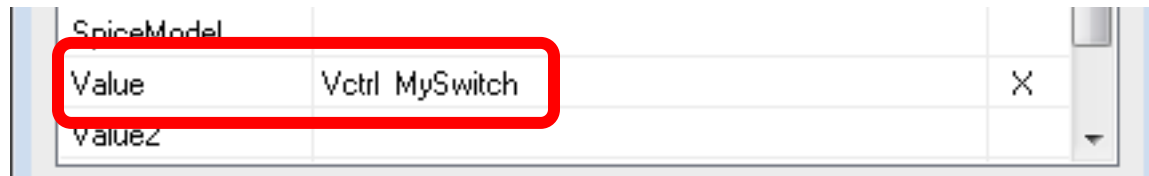
## Current Controlled Switch – Model

- ❖ The name of the schematic component must be changed to correspond to the switch model name.
- ❖ Contrary to the V-switch, the stimulus is not wired to the switch symbol:
  - ❖ The C-switch symbol has only two terminals: the switch's input and output terminals. No control terminal.
  - ❖ The control source is defined by setting the content of the *Value* attribute to read `<Vcontrol> <ModelName>` where
    - `<Vcontrol>` : name of the **voltage** source whose current controls the switch. **Important: Must be a voltage source.**
    - `<ModelName>` : name given to the controlled switch (model name)
  - ❖ As an example:


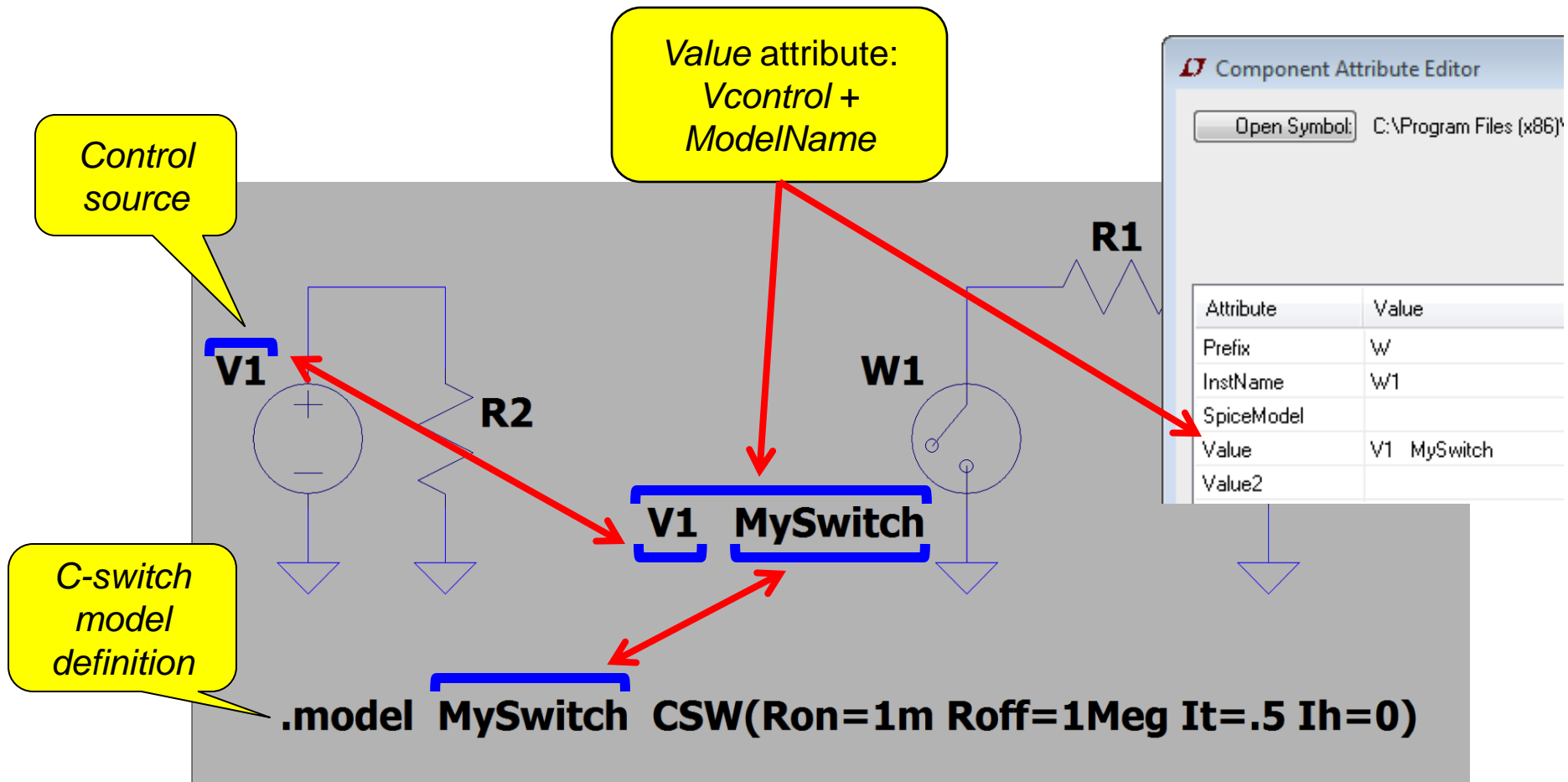
# Current Controlled Switch – Model

- ❖ Schematic example of a current controlled switch:





# Current Controlled Switch – Modes of Operation


- ❖ Like the voltage switch, the CC-switch has three distinct modes of current control depending on the value of the hysteresis current,  $I_h$ :
  - ❖  $I_h = 0A$ : Switch is always completely on or off depending upon whether the control current is above the threshold.
  - ❖  $I_h > 0A$ : it shows hysteresis with trip points at  $I_t - I_h$  and  $I_t + I_h$ .
  - ❖  $I_h < 0A$ : it will smoothly transition between the on and off impedances. The transition occurs between the control currents of  $I_t - I_h$  and  $I_t + I_h$ . The smooth transition follows a low order polynomial fit to the logarithm of the switch's conduction.

# Current Controlled Switch
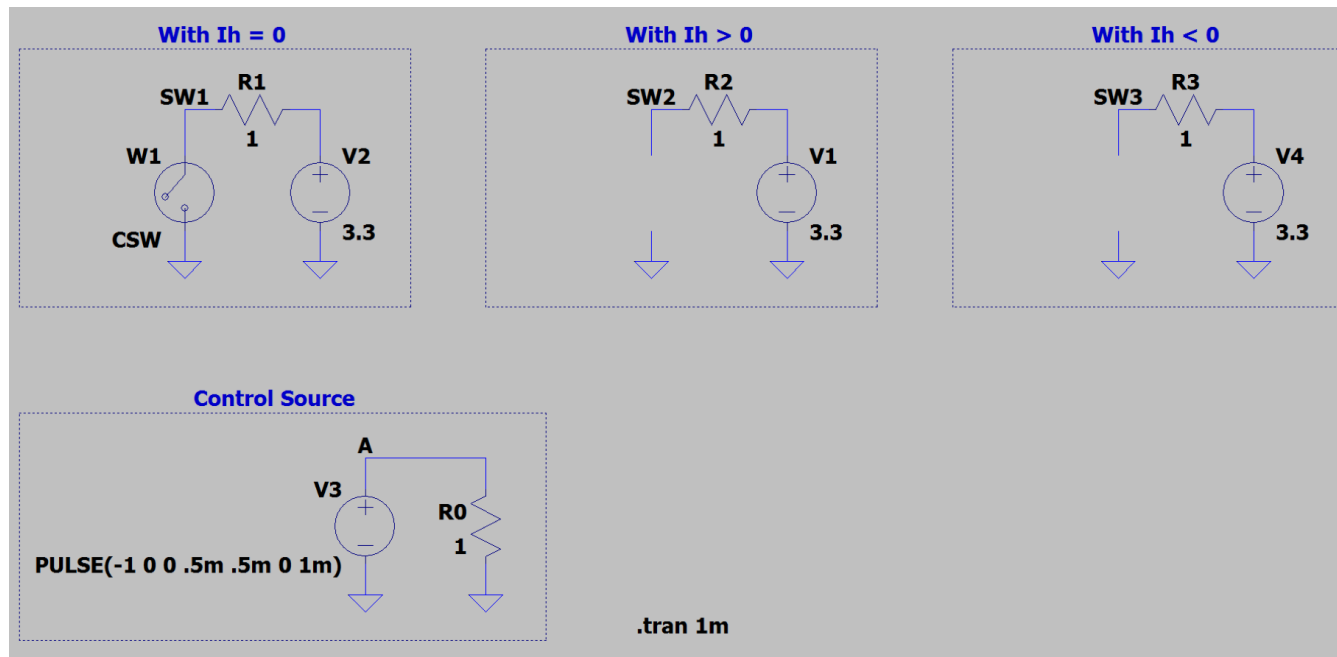
## Hands-on Exercise:



- ❖ Define and use current controlled switches including their control source.
- ❖ Learn to differentiate the different modes of operation of the C-switch.



CswitchLab.asc

# Switches - Application Circuit Examples

- ❖ LT3081 - Linear Regulator current limit
  - ❖ Test the circuit current limiter
- ❖ LTC2954 - Push-Button controller
  - ❖ Replicate the push-button function
  - ❖ Implement a kill switch function
- ❖ LT3954 - LED driver
  - ❖ Open LED circuit response
  - ❖ Emulate a LED cathode short to GND (no dimming)
- ❖ LTC4227 - Dual ideal diode and hot-swap
  - ❖ Check the Ideal diode response to input disconnect
  - ❖ Verify the hot-swap current limiting function



LT3081LDO.asc



LTC2954PBController.asc




LT3954LEDDriver.asc



LTC4227IdealORingAndHotSwap.asc

# ADVANCED TOPICS

To consult at your leisure.

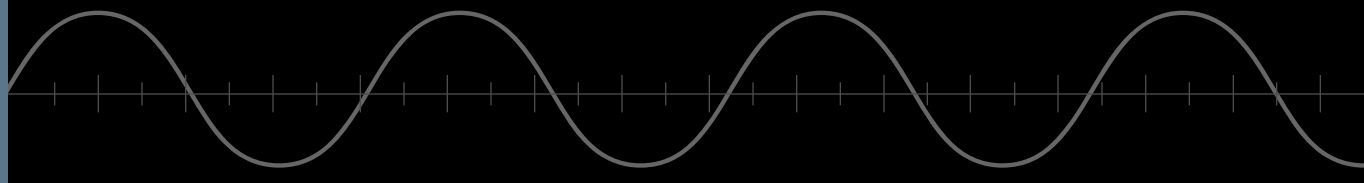

## Voltage Controlled Switch – Level 2 Model

- ❖ The level 2 V-switch model is an advanced version of the level 1 switch with negative hysteresis.

- ❖ The level 2 switch is never completely on or off.

- ❖ The conduction as a function of control voltage  $V_c$  is

$$g(V_c) = \exp(A * \operatorname{atan}((V_c - V_t)/\operatorname{abs}(V_h)) + B)$$

where

- ❖  $A = \log(R_{\text{off}} / R_{\text{on}}) / \pi$

- ❖  $B = \log(1 / (R_{\text{off}} * R_{\text{on}})) / 2$

- ❖ The transition of the level 2 switch to current limit is gradual instead of abrupt. At a fixed control voltage, the I-V curve is given by the equation

$$I(V) = I_{\text{limit}} * \tanh(g(V_c) * V)$$

where  $I_{\text{limit}}$  defaults to 10 amperes for the level 2 switch.


## Voltage Controlled Switch – Level 2 Model

- ❖ The level 2 switch supports the option to conduct in only one direction by specifying either the flag "oneway" or a voltage drop with parameter  $V_{ser}$ .
  - ❖ The transition between forward conduction and reverse open circuit can be specified to be a smooth transition by specifying the parameter  $\epsilon$  to be non-zero.
- ❖ Syntax
  - .model <ModelName> SW(level=2 Ron=< $\Omega$ > Roff=< $\Omega$ > Vt=<V> Vh=<V> Lser=<H> Vser=<V> Ilimit=<A> oneway)*
  - ❖  $V_h$  is always negative
- ❖ The C-Switch does not have a level 2 model.
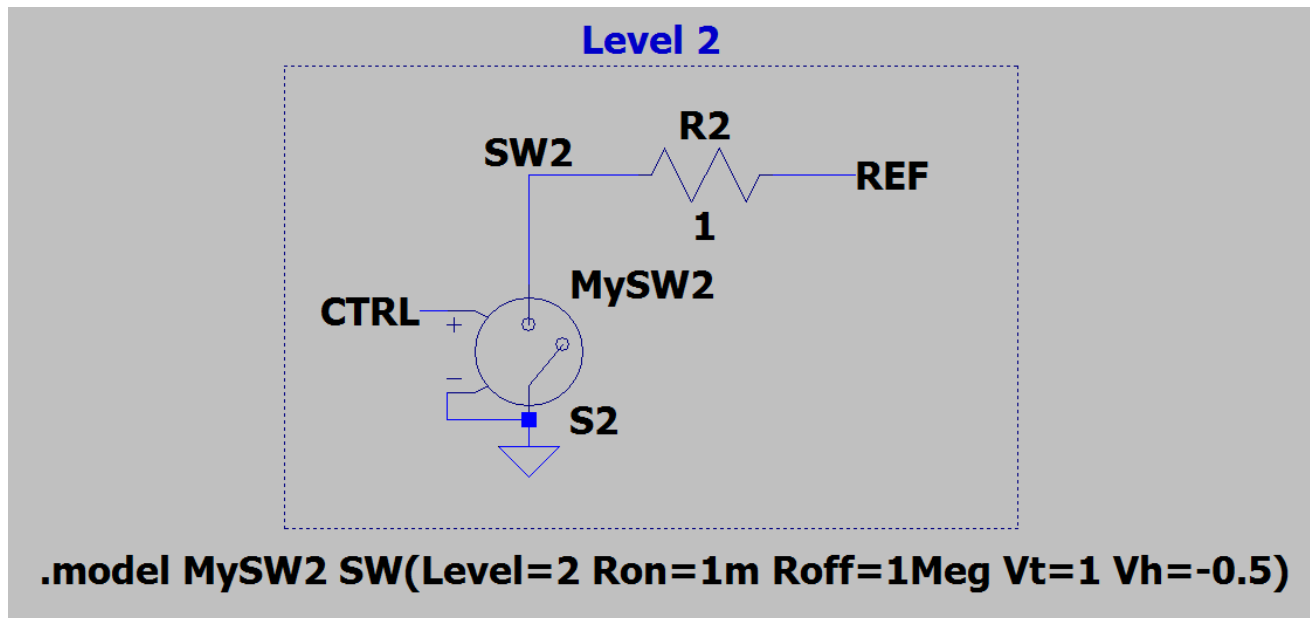
# Voltage Controlled Switch – Level 2 Model

Lab to consult at your leisure:

- ❖ Shows how to define and use level 2 voltage controlled switches.
- ❖ Demonstrates the differences between a level 2 and a level 1 with negative hysteresis V-switch.



VswitchLevel2Solution.asc