



LI IEEE 2024

Louis Diana SMTS


**Switch-Mode Power Supplies (SMPS) Topologies
and Fundamentals**

Agenda

- Power terminology you need to know (Conduction modes and Control methods)
- Non-Synchronous/Synchronous Buck converter operation
- Boost converter operation
- Inverting Buck operation
- 4 switch Buck/Boost operation
- Fly-buck, SEPIC, Flyback, and Forward converter operation
- Brief overview of other converters you may encounter
- What questions to ask
- Efficiency, size, and cost – how do they effect the design

Buck, boost and buck-boost derived topologies

Buck,
forward,
push-pull,
bridge

 


- Forward
- Two switch forward
- Active clamp forward
- Half bridge

$$V_{OUT} = V_{IN} \cdot D \cdot \frac{N_s}{N_p}$$

- Push-pull
- Full bridge
- Phase-shifted full bridge

$$V_{OUT} = V_{IN} \cdot 2 \cdot D \cdot \frac{N_s}{N_p}$$

Boost

 


- Boost topology

On-time duty cycle:
 D

Off-time duty cycle:
 $D' = 1 - D$

Buck-boost,
SEPIC,
flyback

 

- Buck-boost derived topologies
- SEPIC
- Cuk

- Flyback

$$V_{OUT} = V_{IN} \cdot \frac{D}{D'} \cdot \frac{N_s}{N_p}$$

Continuous Vs. Discontinuous conduction mode

 


Fig. 8. - Continuous Mode Waveforms

 


Fig. 9. - Discontinuous Mode

Loop Control Methods (Voltage Mode)


 


Figure 10. - PWM Comparator

 

Loop Control Methods (Peak current mode)

 


Figure 13. - Peak Current Mode Control

Loop Control Methods DCAP with Constant On-Time Modulator

3


Fundamental Components

2. PWM

COMPARATOR

compares V_{FB}

DIRECTLY with V_{REF}

 


3. ON-TIME TIMER

generates on-time proportional to
 V_{in}/V_{out} for pseudo constant frequency operation

 1. ESR combines current information on top of the average output voltage

Non-Synchronous Buck Converter overview

Buck converter makes a lower output voltage than the input voltage



Duty Cycle


$$D = \frac{V_{out} + V_f}{V_{in} + V_f}$$

Q1 FET Voltage

$$V_{Q1} = V_{in} + V_f$$


D1 Diode Voltage

$$V_{D1} = V_{in}$$

 

Synchronous Buck converter overview

 Buck converter makes a lower output voltage than the input voltage



Duty Cycle


$$D = \frac{V_{\text{out}}}{V_{\text{in}}}$$

Q1 FET Voltage

$$V_{Q1} = V_{\text{in}}$$



D1 Diode Voltage

$$V_{Q2} = V_{\text{in}}$$

 


Boost converter Overview

  Boost converter makes a higher output voltage than the input voltage



Inverting Buck-Boost

 Inverting Buck-
Boost converter
makes a negative
output voltage
from a positive
input voltage



Duty Cycle

$$D = \frac{-V_{out} + V_f}{-V_{out} + V_f + V_{in}}$$


Q1 FET Voltage

$$V_{Q1} = V_{in} + V_f - V_{out}$$


D1 Diode Voltage

$$V_{D1} = V_{in} - V_{out}$$


PWM

 


Q1 FET Voltage

 


Q1 FET Current

 


D1 Diode / Q2 FET Voltage

 

D1 Diode / Q2 FET Current

 

L1 Inductor Current

 

Inverting Buck-Boost

 


Figure 2. TPS62120 Inverting Buck-Boost Topology

4 Switch Buck/Boost

 


Figure 24. LM5175 Four-Switch Buck Boost Application Schematic


 


Figure 1. Buck-Boost Converter Schematic

Fly-Buck Converter

 

Duty Cycle


$$D = \frac{V_{out_pri}}{V_{in}}$$

Q1 FET Voltage

$$V_{Q1} = V_{in}$$

D1 Diode Voltage
 
$$V_{D1} = V_{out_sec} + (V_{in} - V_{out_pri}) \cdot \frac{N_s}{N_p}$$



Fly-Buck Converter


 


Figure 1 Split Rail Power Supply Schematic using the Inverting Method.

Sepic Converter

Can buck or boost

 

Duty Cycle

$$D = \frac{V_{out} + V_f}{V_{out} + V_f + V_{in}}$$

Q1 FET Voltage

$$V_{Q1} = V_{in} + V_{out} + V_f + \frac{V_{C1, ripple}}{2}$$

D1 Diode Voltage

$$V_{D1} = V_{in} + V_{out} + \frac{V_{C1, ripple}}{2}$$

 


Figure 1: A coupled-inductor SEPIC converter has two current paths


 


Figure 2: Key waveforms for a continuous-conduction-mode (CCM) SEPIC

Flyback Converter

 

Duty Cycle

$$D = \frac{(V_{out} + V_f) \cdot \frac{N_p}{N_s}}{V_{in} + (V_{out} + V_f) \cdot \frac{N_p}{N_s}}$$


Q1 FET Voltage

$$V_{Q1} = V_{in} + (V_{out} + V_f) \cdot \frac{N_p}{N_s}$$


D1 Diode Voltage

$$V_{D1} = V_{out} + V_{in} \cdot \frac{N_s}{N_p}$$


PWM

 


Q1 FET Voltage

 


Q1 FET Current

 


D1 Diode Voltage

 


D1 Diode Current

 


Np Primary Current

 

Ns Secondary Current

 

Forward Converter

 

Duty Cycle

$$D = \frac{(V_{\text{out}} + V_f)}{V_{\text{in}}} \cdot \frac{N_s}{N_p}$$

Q1 FET Voltage

$$V_{Q1} = 2 \cdot V_{\text{in}} + V_f$$


D1 Diode Voltage

$$V_{D1} = (V_{\text{in}} + V_f) \cdot \frac{N_s}{N_d} - V_f$$


D2 Diode Voltage

$$V_{D2} = V_{\text{in}} \cdot \frac{N_s}{N_p} - V_f$$


ACTIVE CLAMP FORWARD

 


PWM

 


Q1 FET Voltage

 


Q1 FET Current

 


Np Primary Current

 

Ns Secondary Current

 


L1 Inductor Current

 


Various other converters


Push-Pull

 


Half-Bridge

 


Full-Bridge

 

Phase Shifted Full-Bridge

 

LLC Half-Bridge

 

Questions to ask when working on a PS

Design specifications

- $V_{in\max} = 30V$
- $V_{in\min} = 26V$
- $V_{out} = 15V$
- $I_{omax} = 2.8A$
- Switching Frequency = 300khz
- V_{out} ripple = 50mV
- V_{in} ripple = 500mV
- Efficiency > 90%


Power Supply Trades

- Size
- Cost
- Efficiency
- Can you have all 3?


DC/DC Switch-Mode Power Supplies(SMPS)

- The end unless you want to get into the real stuff

Buck design example/discussion terms

 

Voltage-mode buck power stage

 


$$A_{VC} = \frac{V_{IN}}{V_{RAMP}}$$

$$\omega_o = \frac{1}{\sqrt{L \cdot C_{OUT}}}$$


$$Q_o = \frac{R_{OUT}}{\sqrt{L/C_{OUT}}}$$
 
$$\omega_z = \frac{1}{R_{ESR} \cdot C_{OUT}}$$



$$\frac{\hat{v}_{OUT}}{\hat{v}_c} = A_{VC} \cdot \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{Q_o \cdot \omega_o} + \frac{s^2}{\omega_o^2}}$$

Current-mode buck power stage

 

$$R_i = A \cdot R_s$$


$$\omega_z = \frac{1}{R_{ESR} \cdot C_{OUT}}$$

$$A_{VC} \approx \frac{R_{OUT}}{R_i}$$

$$K_m \approx \frac{V_{IN}}{V_{SLOPE}} \quad \text{at } D = 0.5$$


$$\omega_p \approx \frac{1}{C_{OUT} \cdot R_{OUT}}$$

$$\omega_L = \frac{K_m \cdot R_i}{L}$$

 


$$\frac{\hat{v}_{OUT}}{\hat{v}_c} \approx A_{VC} \cdot \frac{1 + \frac{s}{\omega_z}}{\left(1 + \frac{s}{\omega_p}\right) \cdot \left(1 + \frac{s}{\omega_L}\right)}$$

Type I error amplifier

 

 
$$\omega_{EA} = \frac{1}{R_{FBT} \cdot C_{COMP}}$$



$$\frac{\hat{v}_C}{\hat{v}'_{OUT}} \approx -\frac{\omega_{EA}}{s}$$

Type II error amplifier

 


$$A_{VM} \approx \frac{R_{COMP}}{R_{FBT}}$$

$$\omega_{ZEA} = \frac{1}{R_{COMP} \cdot C_{COMP}}$$


$$\omega_{HF} \approx \frac{1}{R_{COMP} \cdot C_{HF}}$$

Assumption: $C_{COMP} \gg C_{HF}$

 

$$\hat{\hat{v}_C} \approx -A_{VM} \cdot \frac{1 + \frac{\omega_{ZEA}}{s}}{1 + \frac{s}{\omega_{HF}}} \approx -\frac{A_{VM} \cdot \omega_{ZEA}}{s} \cdot \frac{1 + \frac{s}{\omega_{ZEA}}}{1 + \frac{s}{\omega_{HF}}}$$

Type II transconductance amplifier

 

$$A_{VM} = K_{FB} \cdot g_m \cdot R_{COMP}$$


$$\omega_{ZEA} = \frac{1}{R_{COMP} \cdot C_{COMP}}$$

$$\omega_{HF} \approx \frac{1}{R_{COMP} \cdot C_{HF}}$$

Assumptions: $C_{COMP} \gg C_{HF}$ & $R_{EA} \gg R_{COMP}$


$$K_{FB} = \frac{R_{FBB}}{R_{FBB} + R_{FBT}}$$

$$A_{OL} = g_m \cdot R_{EA}$$

 

$$\frac{\hat{v}_C}{\hat{v}'_{OUT}} \approx -A_{VM} \cdot \frac{1 + \frac{\omega_{ZEA}}{s}}{1 + \frac{s}{\omega_{HF}}} \approx -\frac{A_{VM} \cdot \omega_{ZEA}}{s} \cdot \frac{1 + \frac{s}{\omega_{ZEA}}}{1 + \frac{s}{\omega_{HF}}}$$

Type III error amplifier

 

$$A_{VM} \approx \frac{R_{COMP}}{R_{FBT}}$$


$$\omega_{ZEA} = \frac{1}{R_{COMP} \cdot C_{COMP}}$$

$$\omega_{FP} = \frac{1}{R_{FF} \cdot C_{FF}}$$

Assumptions: $C_{COMP} \gg C_{HF}$ & $R_{FBT} \gg R_{FF}$

$$\omega_{FZ} \approx \frac{1}{R_{FBT} \cdot C_{FF}}$$
 
$$\omega_{HF} \approx \frac{1}{R_{COMP} \cdot C_{HF}}$$




$$\frac{\hat{v}_c}{\hat{v}'_{OUT}} = -A_{VM} \cdot \frac{\left(1 + \frac{\omega_{ZEA}}{s}\right) \cdot \left(1 + \frac{s}{\omega_{FZ}}\right)}{\left(1 + \frac{s}{\omega_{FP}}\right) \cdot \left(1 + \frac{s}{\omega_{HF}}\right)} = -\frac{A_{VM} \cdot \omega_{ZEA}}{s} \cdot \frac{\left(1 + \frac{s}{\omega_{ZEA}}\right) \cdot \left(1 + \frac{s}{\omega_{FZ}}\right)}{\left(1 + \frac{s}{\omega_{FP}}\right) \cdot \left(1 + \frac{s}{\omega_{HF}}\right)}$$

Buck design example


Power stage
 
$$\frac{\hat{v}_{OUT}}{\hat{v}_C} \approx A_{VC} \cdot \frac{1 + \frac{s}{\omega_Z}}{1 + \frac{s}{Q_o \cdot \omega_o} + \frac{s^2}{\omega_o^2}}$$




Error amplifier
 
$$\frac{\hat{v}_C}{\hat{v}'_{OUT}} \approx -A_{VM} \cdot \frac{\left(1 + \frac{\omega_{ZEA}}{s}\right) \cdot \left(1 + \frac{s}{\omega_{FZ}}\right)}{\left(1 + \frac{s}{\omega_{FP}}\right) \cdot \left(1 + \frac{s}{\omega_{HF}}\right)}$$



Control loop
 
$$\frac{\hat{v}_{OUT}}{\hat{v}'_{OUT}} = \frac{\hat{v}_{OUT}}{\hat{v}_C} \cdot \frac{\hat{v}_C}{\hat{v}'_{OUT}}$$



References

- 1) Under the Hood of Low-Voltage DC/DC Converters - TI Literature Number: SLUP206
- 2) Understanding Buck Power Stages in Switchmode Power Supplies - SLVA057
- 3) Feedback in the Fast Lane Modeling Extending Current-Mode Control in High Frequency Converters by Brian Lynch, Texas Instruments
- 4) Switch-mode power converter compensation made easy – by Robert Sheehan and Louis Diana
- 5) How to avoid design problems by using worst case analysis calculations by Louis Diana
<\\corpserv\public\FAESummit\Analog\ID3.MP4>